




Sistemas de Processamento Digital de Sinais (SPDSina)

XOR phase detector

Consider two square-wave signals with period T . Determine and sketch the static phase detector characteristic of a XOR circuit operating with these signals with amplitude 0 V and 1 V. Generalize for amplitudes V_N e V_P .


Phase detector with a D-type flip-flop

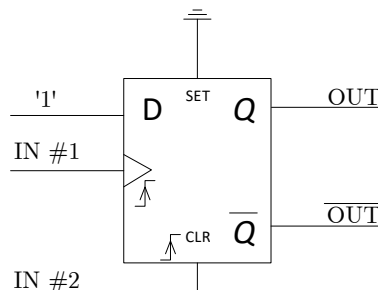Consider the phase detector in the figure which operates with rectangular signals with duty cycles δ_1 and $\delta_2 < \delta_1$, period T and amplitude 0 V and 1 V. Show that its operation is independent of the signals' duty-cycle. Determine and sketch the phase detector static characteristic. What happens when the input signals are switched?




Phase Detectors

XOR

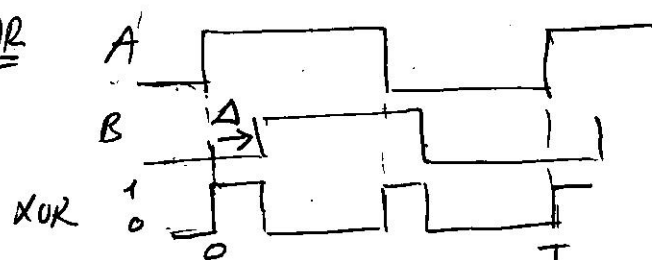

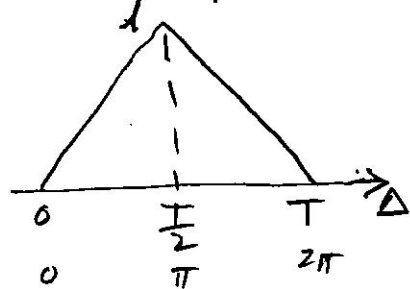
$$\langle \text{XOR} \rangle = \frac{2\Delta}{T}, \quad 0 \leq \Delta \leq \frac{T}{2}$$



For V_P, V_N :

$$0 \leq \Delta \leq \frac{T}{2}$$

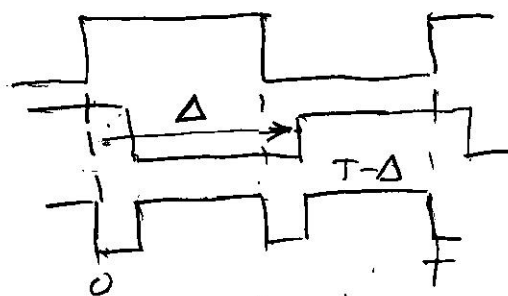


$$\langle \text{XOR} \rangle = \frac{2(T-\Delta)}{T}, \quad \frac{T}{2} < \Delta \leq T$$


$$\begin{aligned} \langle \text{XOR} \rangle &= V_P \frac{2\Delta}{T} + V_N \left(\frac{T-2\Delta}{T} \right) \\ &= V_P \frac{2\Delta}{T} + V_N \left(1 - \frac{2\Delta}{T} \right) \end{aligned}$$

$$\frac{T}{2} < \Delta \leq T$$
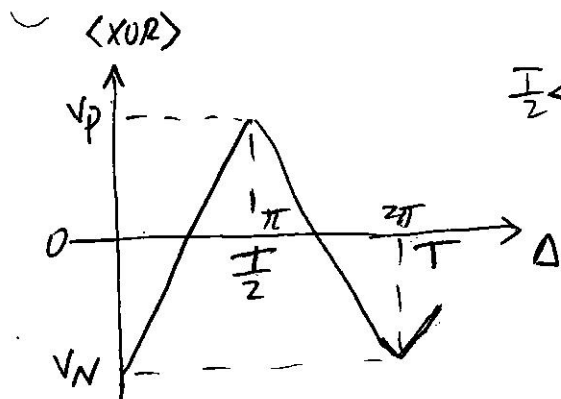
$$\begin{aligned} \langle \text{XOR} \rangle &= V_P \frac{2(T-\Delta)}{T} + V_N \frac{T-2(T-\Delta)}{T} \\ &= V_P 2 \left(1 - \frac{\Delta}{T} \right) + V_N \left(\frac{2\Delta}{T} - 1 \right) \end{aligned}$$



Flip-Flop

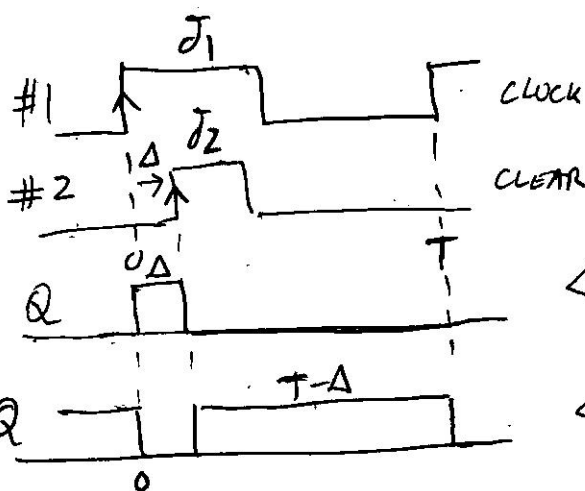

$$\langle Q \rangle = \frac{\Delta}{T}, \quad 0 \leq \Delta \leq T$$

$$\langle Q \rangle = \frac{T-\Delta}{T} = 1 - \frac{\Delta}{T}, \quad 0 \leq \Delta \leq T$$

#1 and #2 switched

Because both clock and clear inputs are edge-triggered, the operation is only sensitive to positive-going transitions. Therefore it does not depend on either σ_1 or σ_2 (duty-cycle).

The available phase is 2π because the detector only has one slope, either positive ($K_D > 0$) or negative ($K_D < 0$) when the inputs are switched.

The characteristic $\langle Q \rangle$ is periodic with the period equal to 2π .

Need to be careful about PLL return gain, $\lambda > 0$!

